

# ECT201 SOLID STATE DEVICES

## COURSE COMPLETION PROJECT

Submitted By:

Jose C S

S3 EC-B

Roll Number:27

University Register Number: KNR23EC053

# MOS PROJECT

*1. Draw the output characteristics ( $I_{ds}$  vs  $V_{ds}$  for different  $V_{gs}$  values) of a N type enhancement mode MOSFET. Draw its transfer characteristics ( $I_{ds}$  vs  $V_{gs}$  for different  $V_{ds}$  values).*

## PROGRAM :

```
* MOSFET Id-Vd plot *
.include "mosmodel.txt"
* Drain voltage source
vd d 0 dc=1.8
* Gate voltage source
vg g 0 dc=0
* Source and substrate are grounded
vs s 0 dc=0
vb b 0 dc=0
* MOSFET model
m1 d g s b CMOSN W=10e-6 L=180e-9
* Sweep drain voltage and gate voltage
.dc vd 0.0 1.8 0.01 vg 0.4 1.8 0.4
.control
run
* Plot settings
set color0=white
set color1=black
set color2=red
set color2=brown
set xbrushwidth=5
plot i(vs)
.endc
.end

* NMOS Id-Vg plot *
.include "mosmodel.txt"
* Drain voltage source
vd d 0 dc=0
* Gate voltage source
vg g 0 dc=0
* Source and substrate are grounded
vs s 0 dc=0
vb b 0 dc=0
```


```

* MOSFET model
m1 d g s b CMOSN W=10e-6 L=180e-9
* Sweep gate voltage and drain voltage
.dc vg 0 1.0 0.01 vd 0.05 1.8 1.75
.control
run
* Plot settings
set color0=white
set color1=black
set color2=red
set color2=brown
set xbrushwidth=5
plot i(vs)
.endc
.end


```

WAVE FORM :

Ids V/s Vds :

 

Ids V/s Vgs:

 

## Output and Transfer Characteristics of an N-Type Enhancement Mode MOSFET

### Output Characteristics ( IDS vs. VDS for Different VGS Values)

#### 1. Description:

- The output characteristics graph shows how the drain current  $I_{DS}$  changes with the drain-source voltage  $V_{DS}$  for various gate-source voltages  $V_{GS}$ .
- When  $V_{GS}$  is increased above the MOSFET's threshold voltage  $V_{TH}$   $I_{DS}$  rises, reflecting the MOSFET turning on.
- Each  $V_{GS}$  value produces a separate curve, with  $I_{DS}$  eventually saturating for higher  $V_{DS}$  values.

#### 2. Key Points:

- The MOSFET remains off, with  $I_{DS}=0$ , until  $V_{GS}$  surpasses  $V_{TH}$ .
- After crossing the threshold,  $I_{DS}$  initially rises linearly with  $V_{DS}$ , entering the saturation region where it then levels off.

- Higher VGS values create distinct curves, showing greater IDS values as VGS increases.

### Transfer Characteristics IDS vs. VGS for Different VDS Values)

#### 1. Description:

- The transfer characteristics graph illustrates how  $I_{DS}$  varies with  $V_{GS}$  for a set of constant  $V_{DS}$  values.
- This plot shows the sensitivity of  $I_{DS}$  to changes in  $V_{GS}$ , especially as different  $V_{DS}$  levels are applied.

#### 2. Key Points:

- At low VGS, IDS remains close to zero until VGS exceeds VTH.
- Once VGS goes beyond VTH, IDS increases sharply, signifying the device's transition from cutoff to saturation.
- Beyond a certain point, IDS plateaus, indicating that the MOSFET has reached saturation.

### Summary of Results:

#### • Output Characteristics:

- Each curve shows that as VGS rises, the peak IDS also increases, with saturation occurring at progressively higher VDS levels for each VGS value.

#### • Transfer Characteristics:

- The graph indicates a sharp increase in IDS as VGS rises above VTH, with the curves' shapes varying slightly based on the VDS applied.

*2. Draw the output characteristics ( $I_{ds}$  vs  $V_{ds}$  for different  $V_{gs}$  values) of a P type enhancement mode MOSFET. Draw its transfer characteristics. ( $I_{ds}$  vs  $V_{gs}$  for different  $V_{ds}$  values).*

PROGRAM :

\* PMOS Id-Vd plot \*

\* include the mosmodel.txt in the same folder

```

.include "mosmodel.txt"
* drain voltage source
vd d 0 dc=0
* gate voltage source  vg g 0 dc=0
* source and substrate are grounded  vs s 0 dc=0  vb b 0 dc=0
* p mosfet model name is same as that given in the model file  m1 d g s b CMOSF
  W=10e-6 L=180e-9
* run drain voltage first and then sweep gate voltage to get the family of curves
.dc vd -1.8 0.0 0.01 vg -1.8 -0.0 0.4
.control
run
*set background color as white, grid lines black, plot red and width of the
line=10 set color0=white set color1=black
set color2=red
set color2=brown
set xbrushwidth=5
plot -i(vs)
.endc
.end

```


```

* pmos: Id-Vg plot *
* include the mosmodel.txt in the same folder
.include "mosmodel.txt"
* drain voltage source
vd d 0 dc=0


* gate voltage source  vg g 0 dc=0
* source and substrate are grounded  vs s 0 dc=0  vb b 0 dc=0
* p mosfet model name is same as that given in the model file  m1 d g s b CMOSF
  W=10e-6 L=180e-9
* run gate voltage first and then sweep drain voltage to get the family of curves
.dc vg -1.8 0 0.01 vd -1.8 -0.05 1.5
.control
run
*set background color as white, grid lines black, plot red and width of the
line=10 set color0=white set color1=black set color2=red set color2=brown
set xbrushwidth=5 plot -i(vs)
.endc
.end

```

WAVE FORM: ( $I_d$  V/S  $V_d$ ):

 

$I_d$  v/s  $V_{gs}$  :

 

## **Output and Transfer Characteristics of a P-Type Enhancement Mode MOSFET**

### **1. Description:**

- The output characteristics graph shows the drain current  $I_{ds}$  plotted against the drain-source voltage  $V_{ds}$  for different gate-source voltages  $V_{gs}$  in a P-type enhancement mode MOSFET.
- As  $V_{gs}$  becomes more negative,  $I_{ds}$  increases, indicating the MOSFET turning on.

### **2. Key Points:**

- The MOSFET remains off, with  $I_{ds}$  at 0, until  $V_{gs}$  falls below the threshold voltage (a negative threshold).
- As  $V_{gs}$  is made more negative,  $I_{ds}$  starts increasing, showing that the device is active.
- Each  $V_{gs}$  value creates a distinct output curve, with higher  $I_{ds}$  values observed as  $V_{gs}$  becomes more negative.

## **Transfer Characteristics ( $I_{ds}$ vs. $V_{gs}$ for Different $V_{ds}$ Values)**

### **1. Description:**

- The transfer characteristics graph shows how  $I_{ds}$  varies with gate-source voltage  $V_{gs}$  when different fixed values of  $V_{ds}$  are applied.
- This plot highlights how  $I_{ds}$  changes with  $V_{gs}$  for a set  $V_{ds}$  value.

### **2. Key Points:**

- At less negative  $V_{gs}$ ,  $I_{ds}$  is close to zero until  $V_{gs}$  surpasses the negative threshold.
- As  $V_{gs}$  becomes more negative,  $I_{ds}$  rises rapidly, marking the transition of the P-MOSFET from cutoff to saturation.
- Eventually,  $I_{ds}$  reaches a steady maximum, illustrating the MOSFET's saturation.

## **Summary of Results:**

- **Output Characteristics:**



- The graph shows that as  $V_{gs}$  becomes more negative,  $I_{ds}$  increases, with each curve indicating a specific  $V_{ds}$  value.
- **Transfer Characteristics:**
  - The plot reveals a rapid rise in  $I_{ds}$  as  $V_{gs}$  becomes more negative, with curve shapes depending on the  $V_{ds}$  levels applied.

*3. Create an CMOS inverter using n-type and p-type enhancement MOSFETs and show that for a pulse input the circuit behaves like an inverter (NOT gate).*

#### **PROGRAM:**


```
* Inverter Transient *
.include "mosmodel.txt"
* Supply voltage
v1 vdd 0 dc=1.8
* Pulse input source
v2 in 0 pulse 0 1.8 1u 1u 1u 100u 200u
* CMOS inverter (N-MOSFET and P-MOSFET)
mn out in 0 0 CMOSN W=1u L=180n
mp out in vdd vdd CMOSP W=2u L=180n
* Transient analysis for 500µs to observe at least two pulses
.tran 10n 500u
.control
run
* Plot settings
set color0=white
set color1=black
set color2=red
set color2=brown
set xbrushwidth=5
plot v(in)
```


plot v(out)

.endc

.end

WAVE FORM:

 

 

## CMOS Inverter Simulation

### Objective:

To design a CMOS inverter using complementary n-type and p-type enhancement MOSFETs and verify its operation as an inverter (NOT gate) through pulse input testing.

### Circuit Description:

- The inverter is constructed using a combination of one n-type MOSFET (MN) and one p-type MOSFET (MP), configured to produce an inverted output.
- A pulse signal is applied to the input, and the resulting output is monitored to verify the inverter's functionality.

### Simulation Program:

1. **Power Supply:**
  - A DC supply voltage (Vdd) of 1.8V is applied.
2. **Input Source:**

- A pulse voltage source (V2) is defined with a range of 0V to 1.8V, pulse width of 1 $\mu$ s, and a period of 200 $\mu$ s.

### 3. MOSFET Definitions:

- **N-Type MOSFET (MN)** : Connected to pull the output down to ground.
- **P-Type MOSFET (MP)** : Connected to pull the output up to Vdd.

### 4. Transient Analysis:

- The transient analysis is set to run for 500  $\mu$ s with a time interval of 10 ns, allowing for observation of at least two pulse cycles in the output response.

#### Key Simulation Details:

- **Input Pulse Behavior:** The input toggles between 0V and 1.8V, mimicking a digital signal.
- **Expected Output Behavior:** The output should be inversely related to the input: when the input voltage is high (1.8V), the output should be low (0V), and vice versa.

#### Expected Results:

- **Output Voltage Behavior:** The output voltage (v(out)) should exhibit an inverted response to the input voltage (v(in)).
- **Inversion Confirmation:** The output should drop to low when the input is high, and rise to high when the input is low, confirming proper inverter action.

#### Visual Output:

- The simulation will display the input and output voltage waveforms over time, visually verifying the inverter's correct operation.